

Computer-Aided VLSI System Design

Homework 4: IoT Data Filtering

Graduate Institute of Electronics Engineering, National Taiwan University



NTU GIEE




Goals

- In this homework, you will learn
 - Generate patterns for testing
 - Optimizing the trade-off between power consumption, operating frequency, and area
 - Use primetime to estimate power
 - Learn to design an architecture for processing data with long bit lengths
 - Learn to efficiently access the look-up table and accelerate its throughput




Introduction

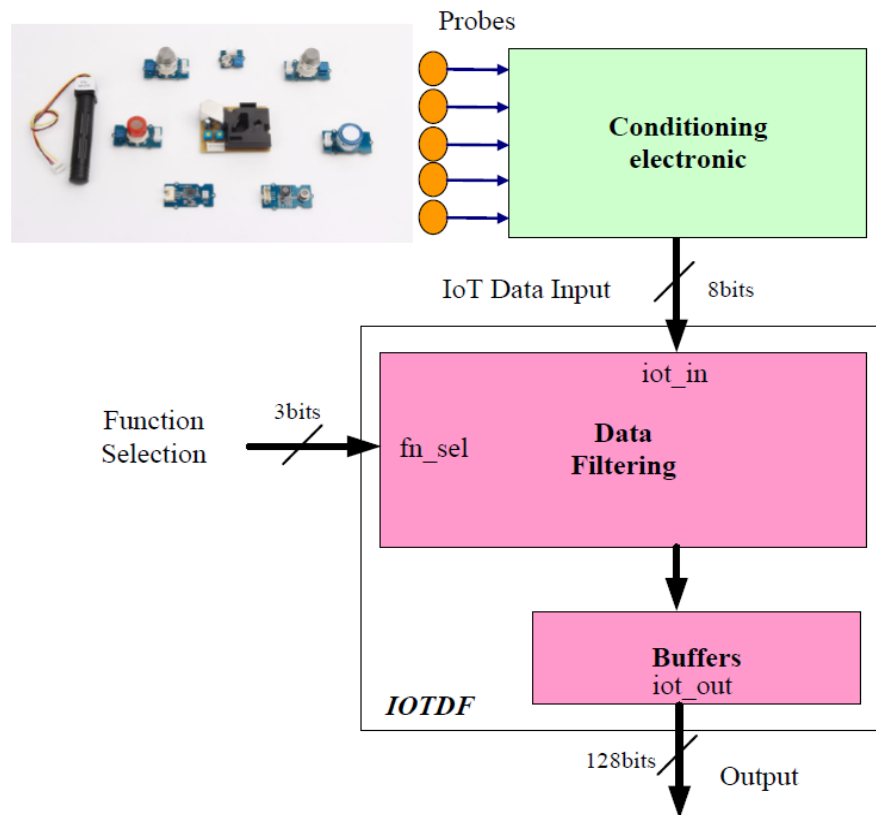- You are asked to design a IoT Data Filtering (IOTDF), which can processor large IoT data from the sensors, and output the result in real-time [1]






Block Diagram

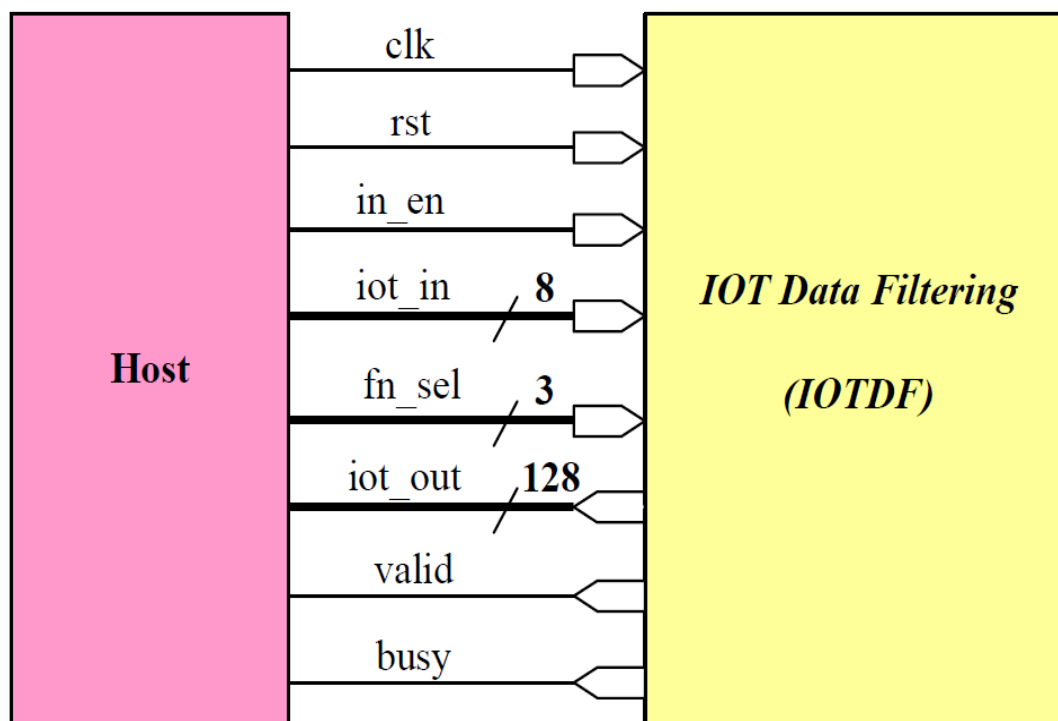




Design Description

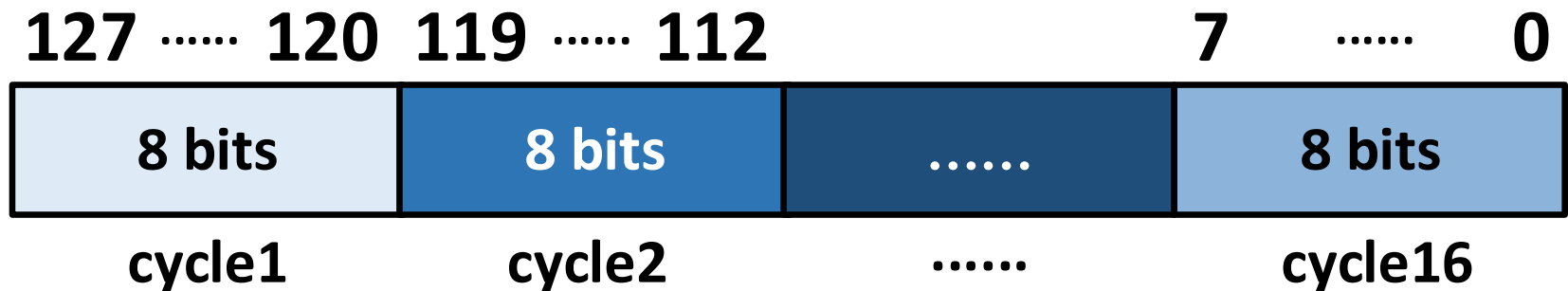- The sensor data is a 128-bit unsigned data, which is divided in 16 8-bit partial data for IOTDF fetching.
- Only 60 data are required to fetch for each function simulation.



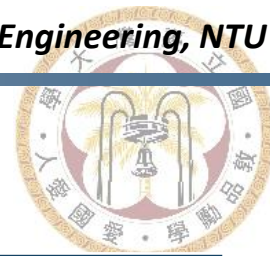


Input/Output

Signal Name	I/O	Width	Simple Description
clk	I	1	Clock signal in the system (positive edge trigger). All inputs are synchronized with the positive edge clock. All outputs should be synchronized at clock rising edge
rst	I	1	Active high asynchronous reset.
in_en	I	1	Input enable signal. When busy is low, in_en is turned to high for fetching new data. Otherwise, in_en is turned to low if busy is high. If all data are received, in_en is turned to low to the end of the process.
iot_in	I	8	IoT input signal. Need 16 cycles to transfer one 128-bit data. The number of data is.
fn_sel	I	3	Function Select Signal. There are 5 functions supported in IOTDF. For each simulation, only 1 function is selected for data processing.
iot_out	O	128	IoT output signal. One cycle for one data output.
busy	O	1	IOTDF busy signal (explained in description for in_en)
valid	O	1	IOTDF output valid signal Set high for valid output



Specification (1)

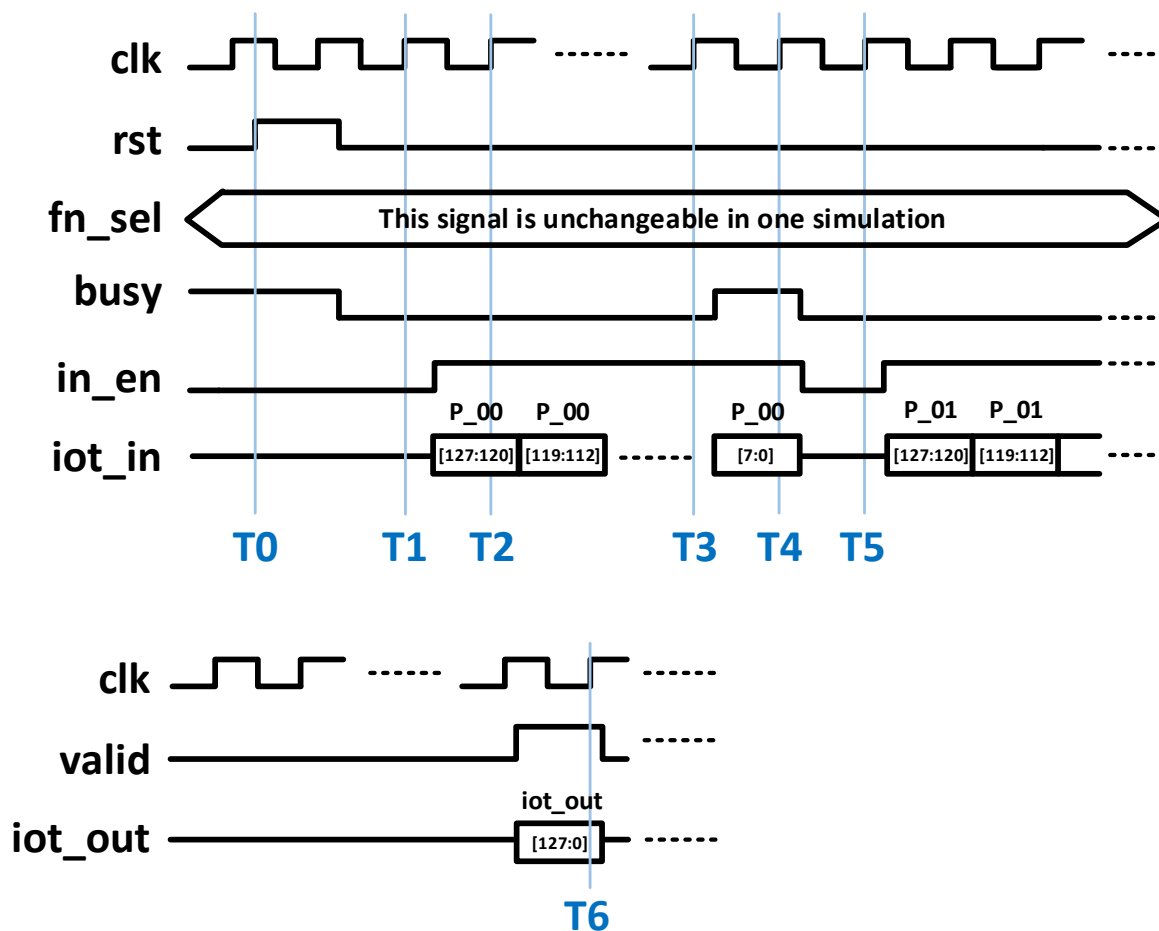
- IOTDF is initialized between $T_0 \sim T_1$.





Specification (2)

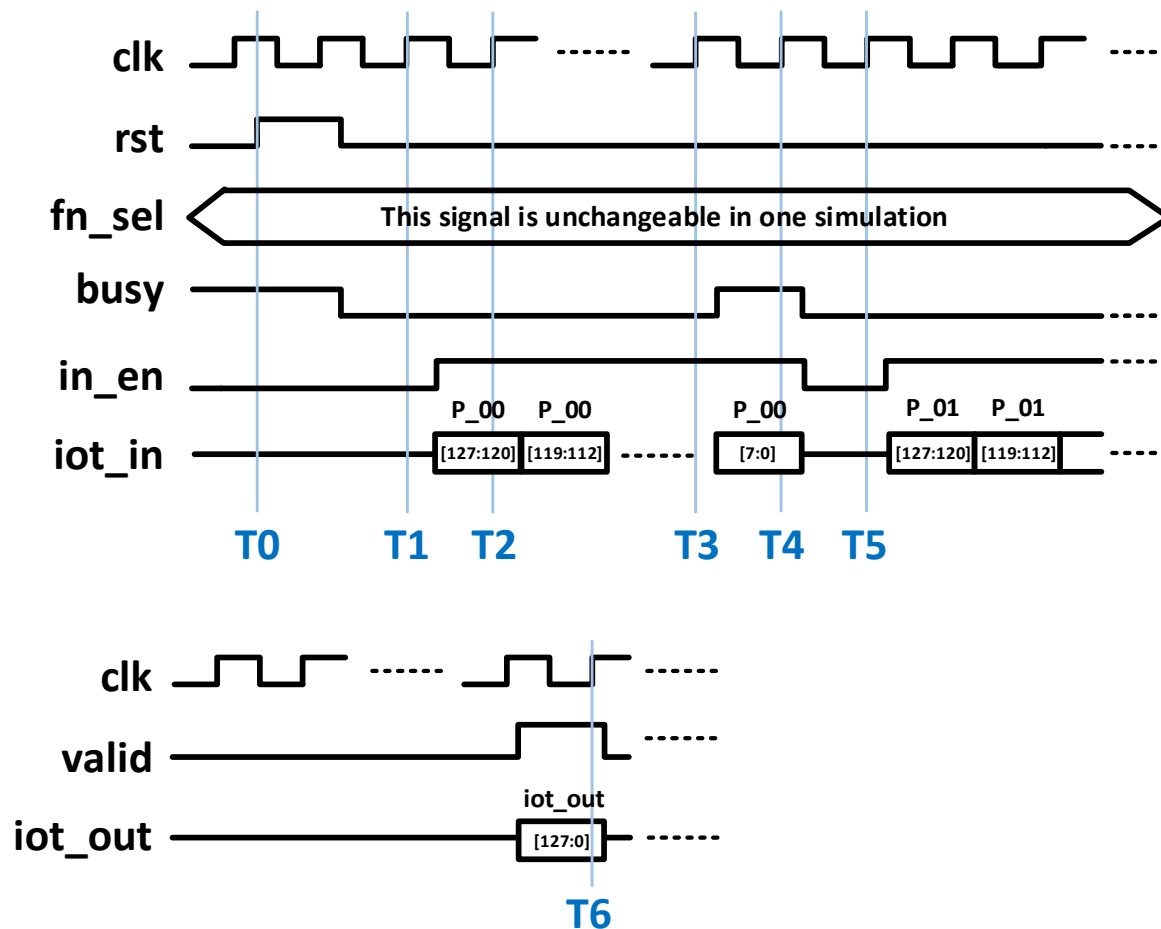
- in_en is set to high and start to input IoT data P_00[127:120] if busy is low at T1.






Specification (3)

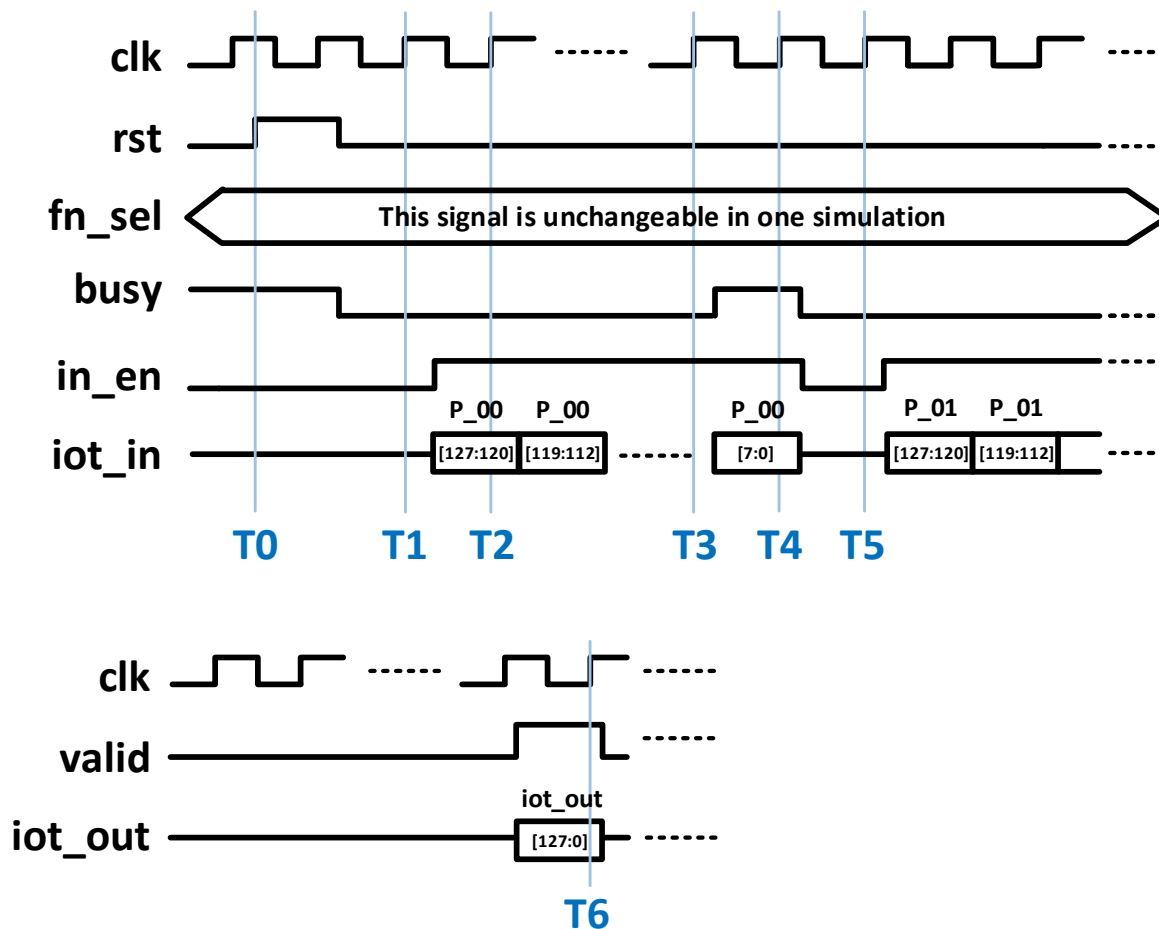
- in_en is kept to high and input IoT data P_00[119:112] if busy is low at T2.



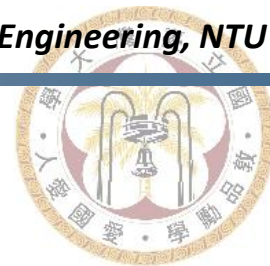

Specification (4)

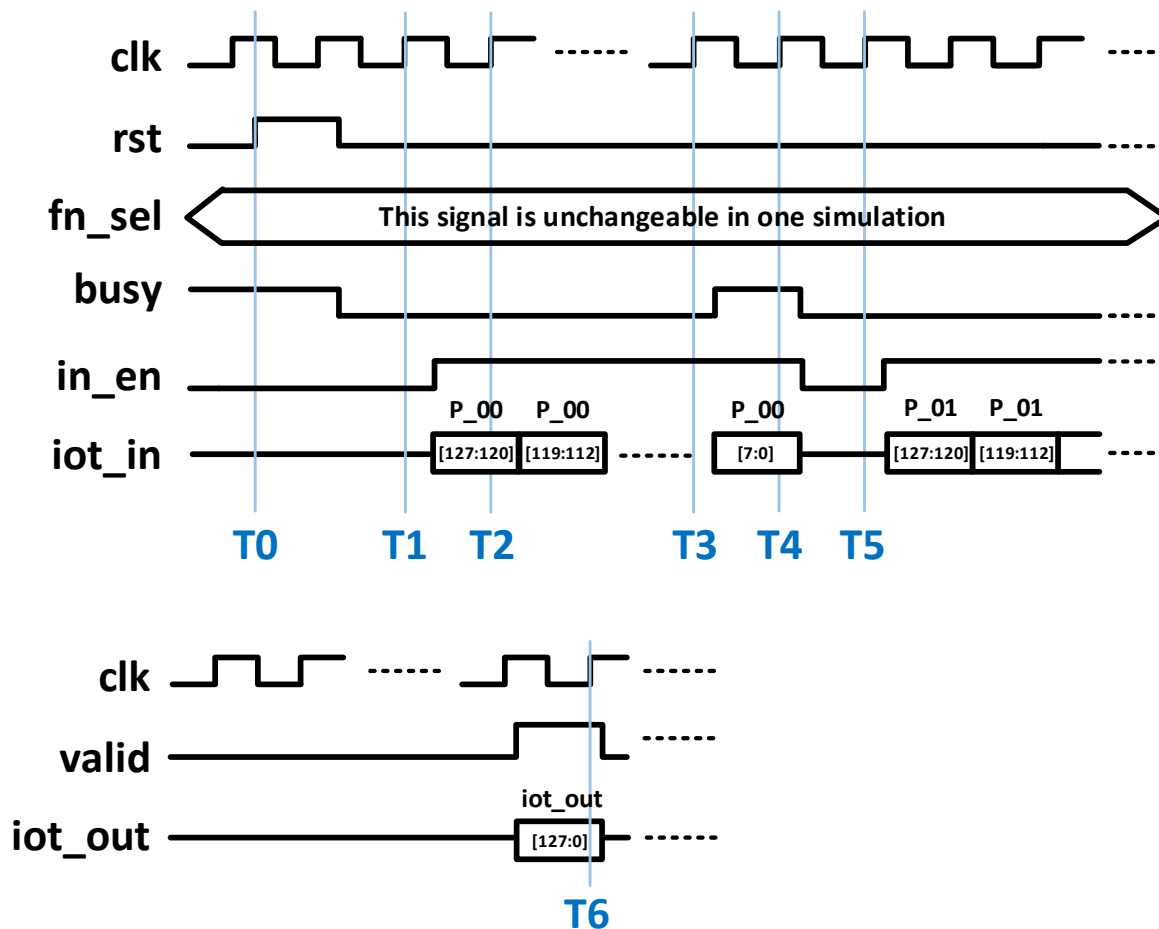
- in_en is kept to high and input IoT data P_00[7:0] if busy is low at T3.





Specification (5)

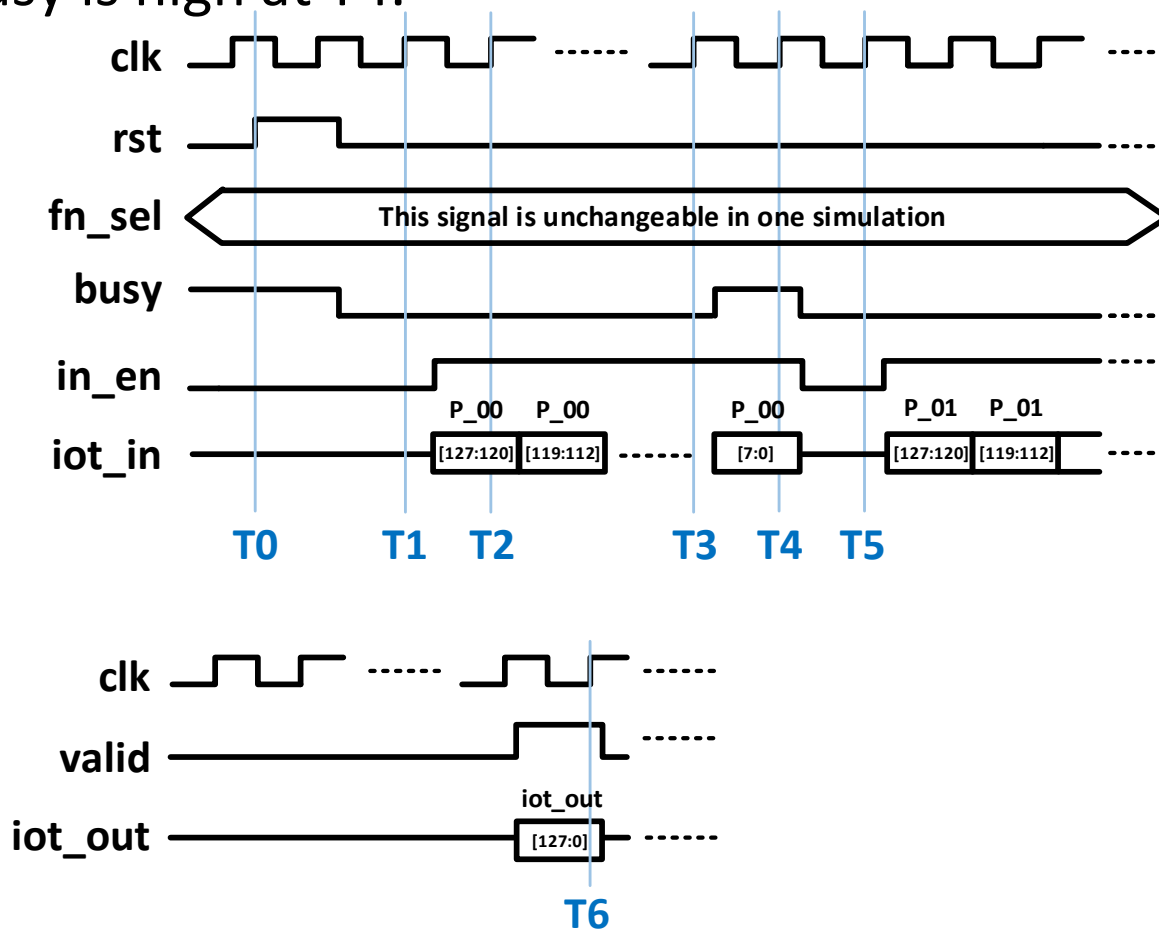
- in_en is set to low and IoT data is set to 0 (stop streaming in data) if busy is high at T4.





Specification (6)

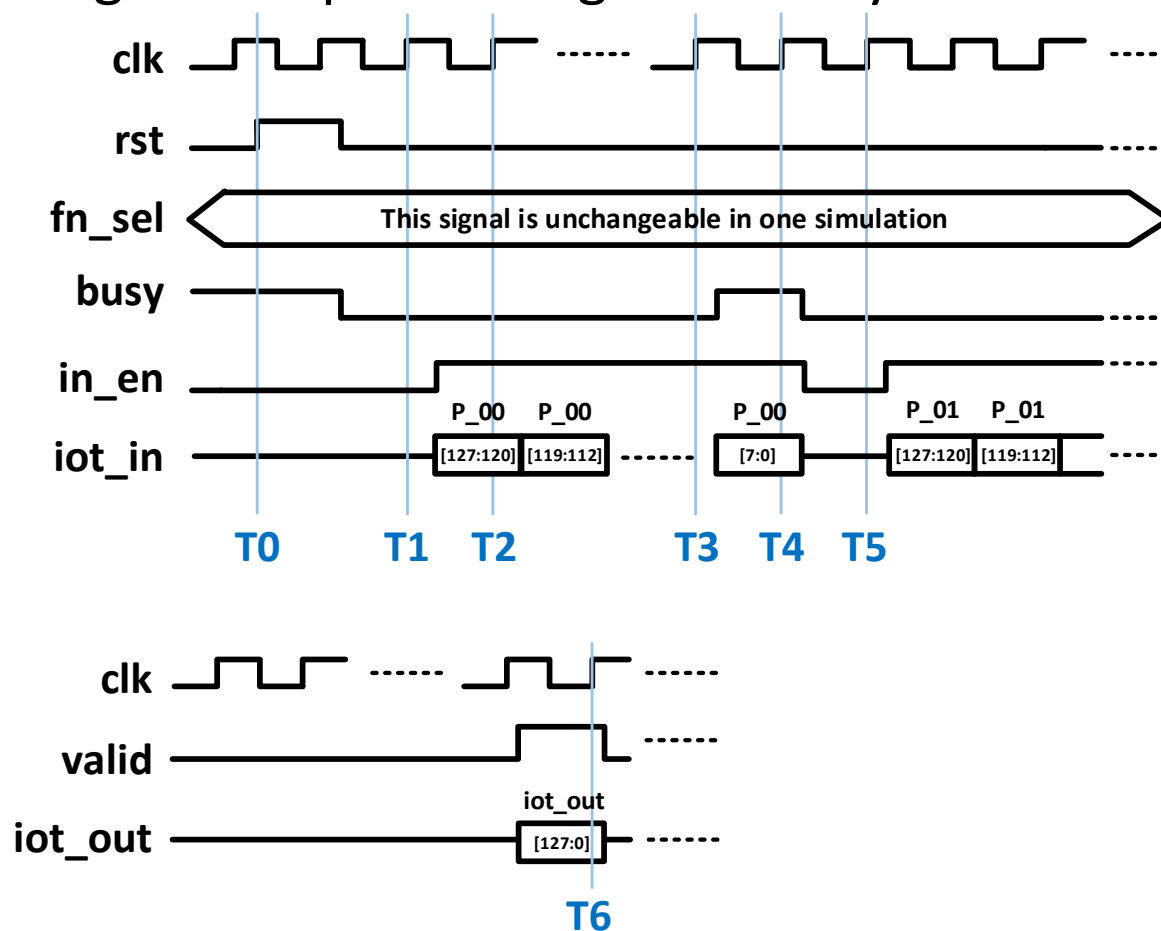
- There are 16 cycles between T1~T4 for one IoT data. You can set busy to high to stop streaming in data if you want.






Specification (7)

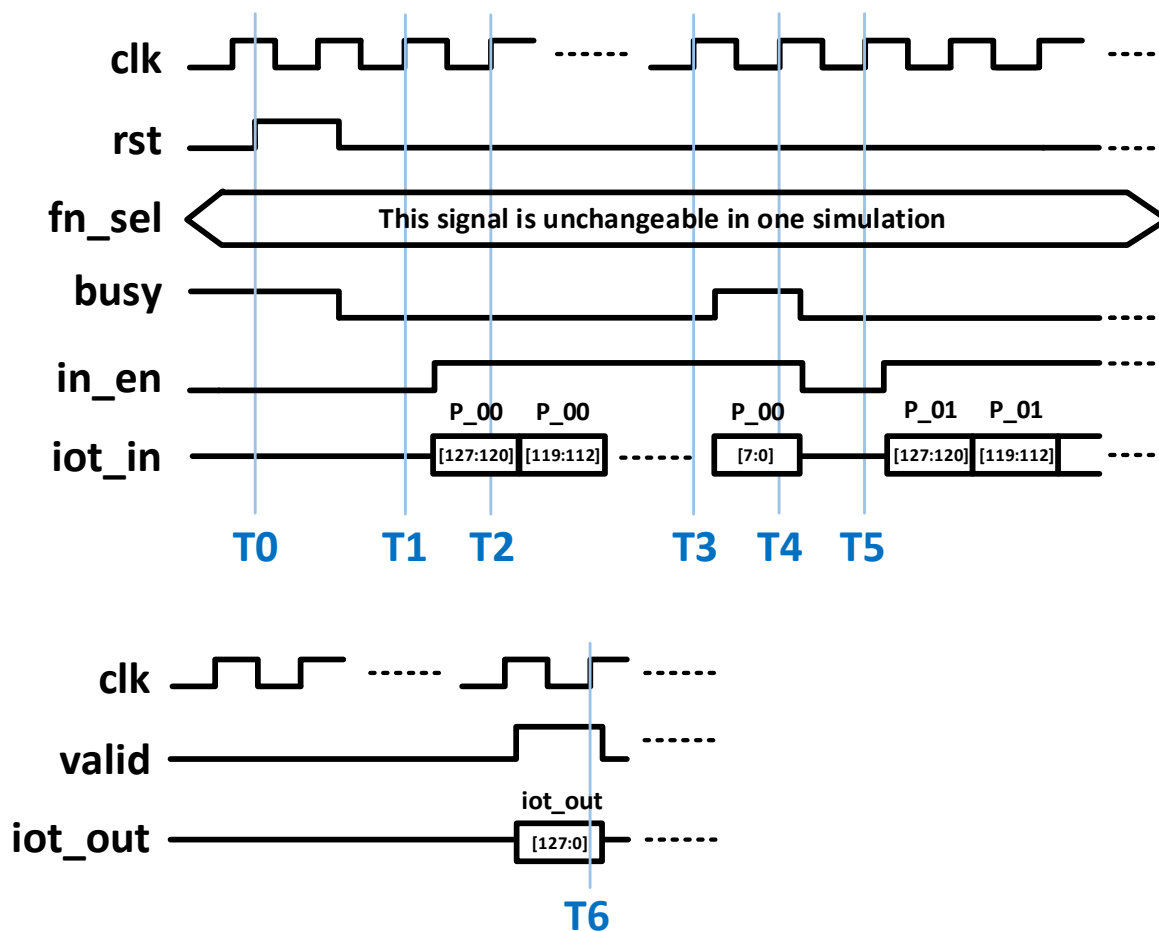
- You have to set valid to high if you want to output iot_out.



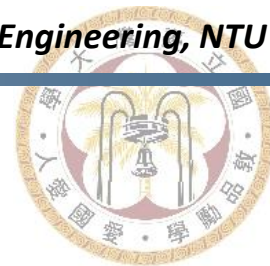

Specification (8)

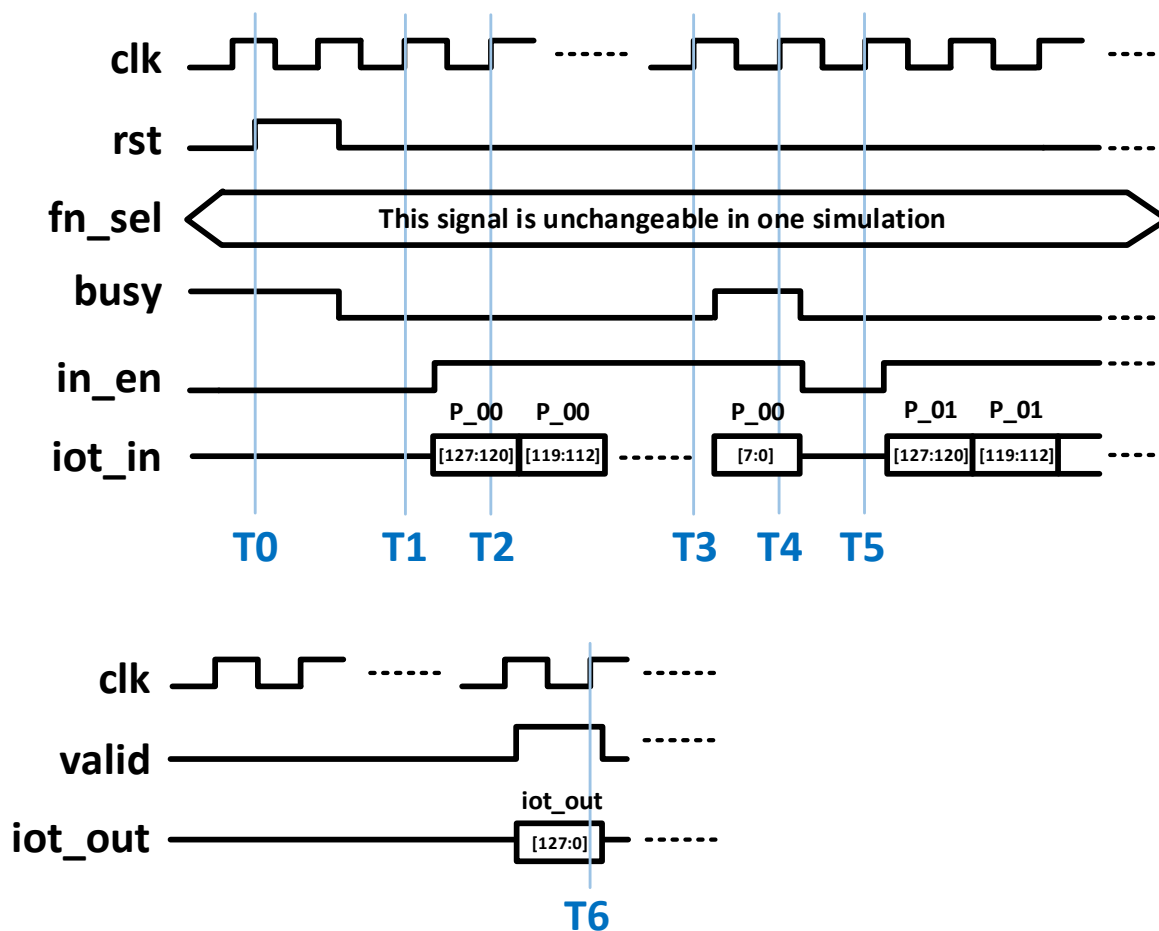- The whole processing time can't exceed 1000000 cycles.






Functions

	Fn_sel	Functions
F1	3'b001	Encrypt(N)
F2	3'b010	Decrypt(N)
F3	3'b011	CRC_gen(N)
F4	3'b100	Bin2Gray(N)
F5	3'b101	Gray2Bin(N)



F1: Encrypt(N)

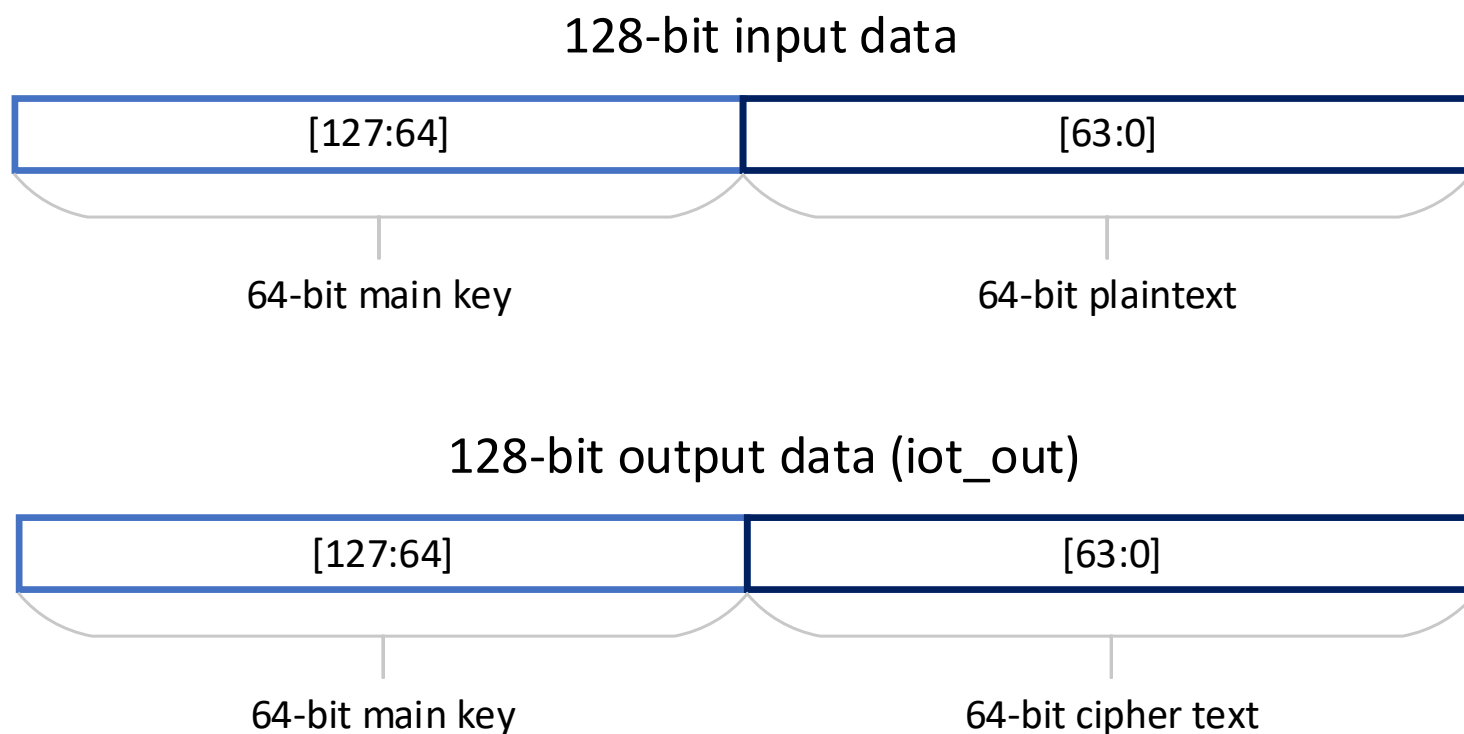- Use the DES algorithm to encrypt 64-bit data [2]







Data Encryption Standard (DES)

- Development
 - IBM's creation, 1970s
 - Adopted by NIST in 1977
- Application
 - Prevailing encryption for years
 - Basis for modern ciphers
- Security
 - Susceptible to brute-force
 - Superseded by Advanced Encryption Standard (AES)



DES Workflow

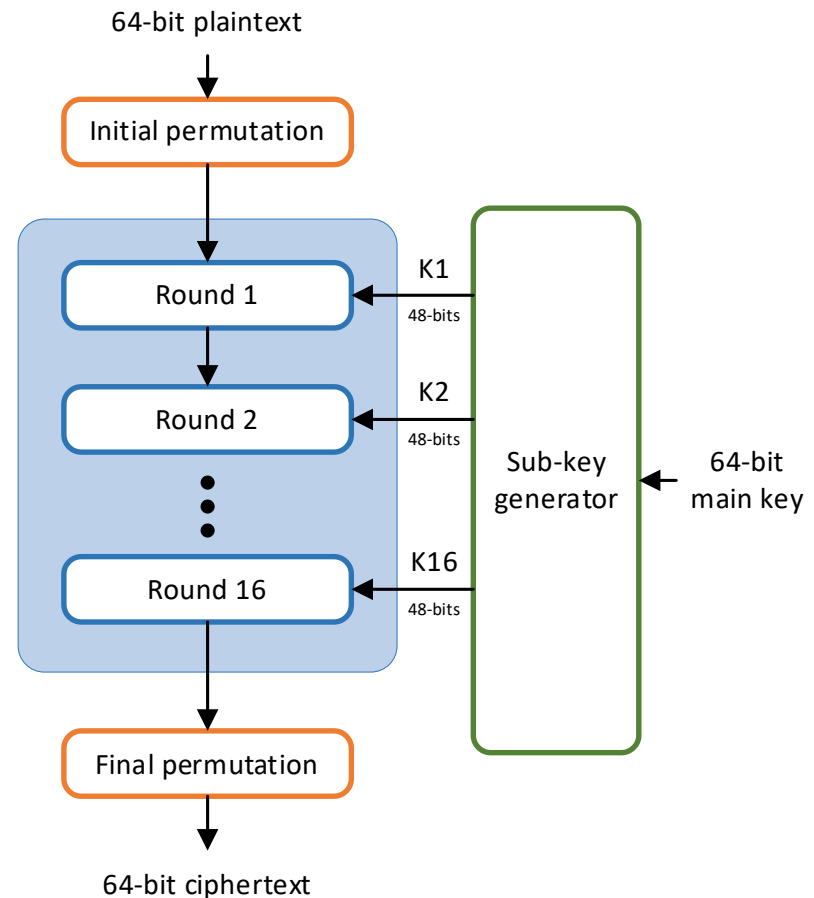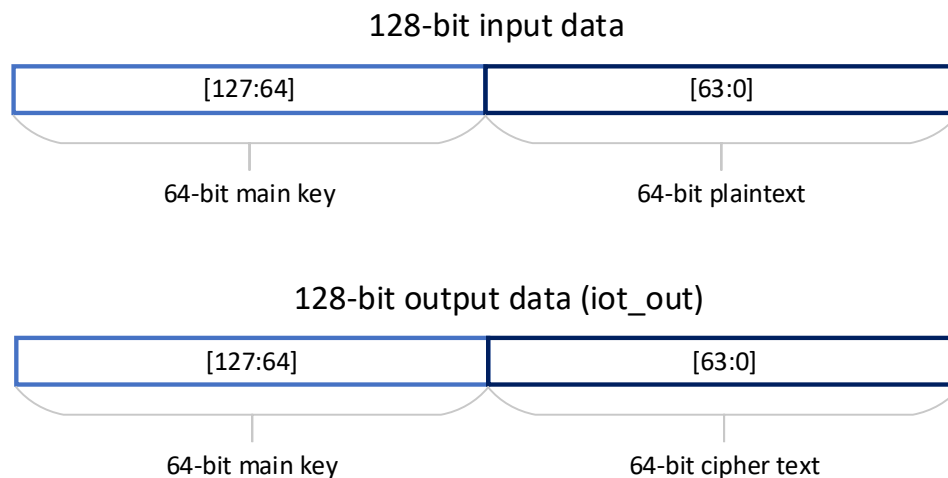- Require 16 rounds of encryption
- Each round needs a different sub-key
- The orange box represents a LUT
- Final permutation is the inverse of the initial permutation






Permutation Table


- Excel file for the Permutation Table is located in the "permutations" folder
- Name of the Excel file matches the table name
 - Ex: Initial permutation corresponds to Initial_permutation.xlsx

	A	B
1	Output index	Input index
2	55	7
3	54	15
4	53	23
5	52	31
6	51	39
7	50	47
8	49	55
9	48	63
10	47	6
11	46	14
12	45	22
13	44	30

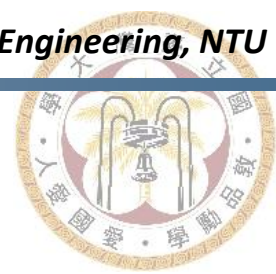

Details Of Key Generator

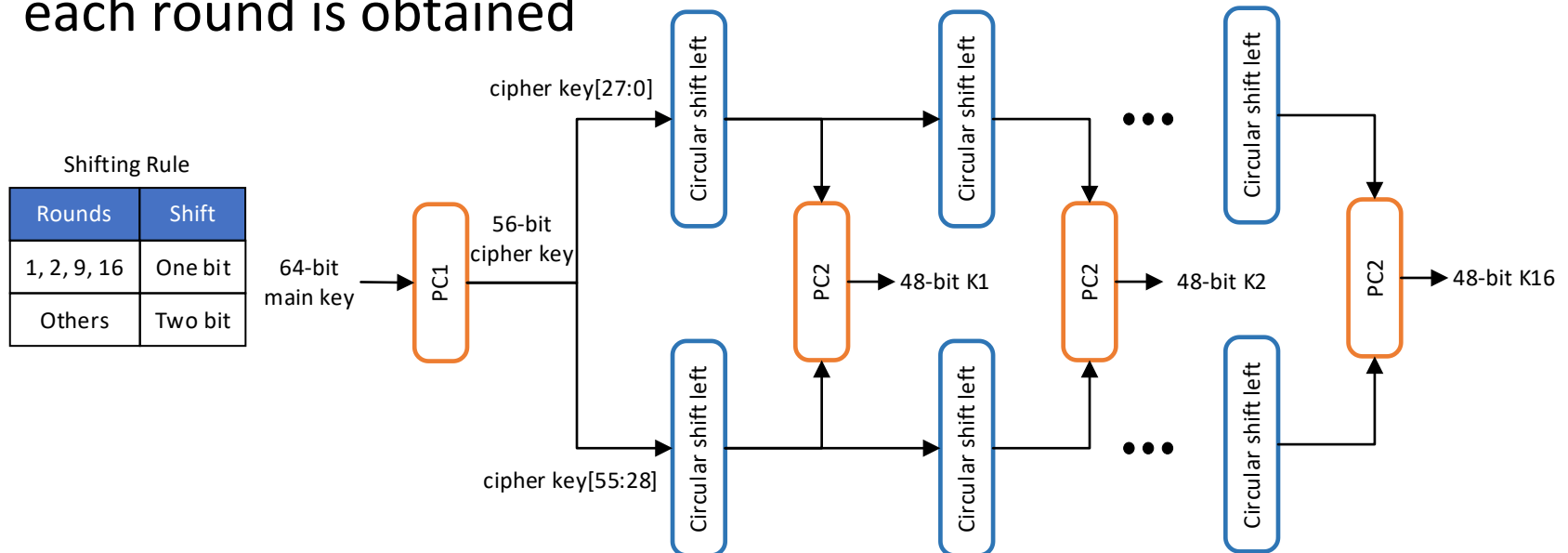
- Main key is processed through the PC1 LUT to form the cipher key, then split into left and right halves for circular shift left
- Each round has different shift amount, following the shifting rule
- After passing through the PC2 LUT, the sub-key required for each round is obtained






Details Of Each Round

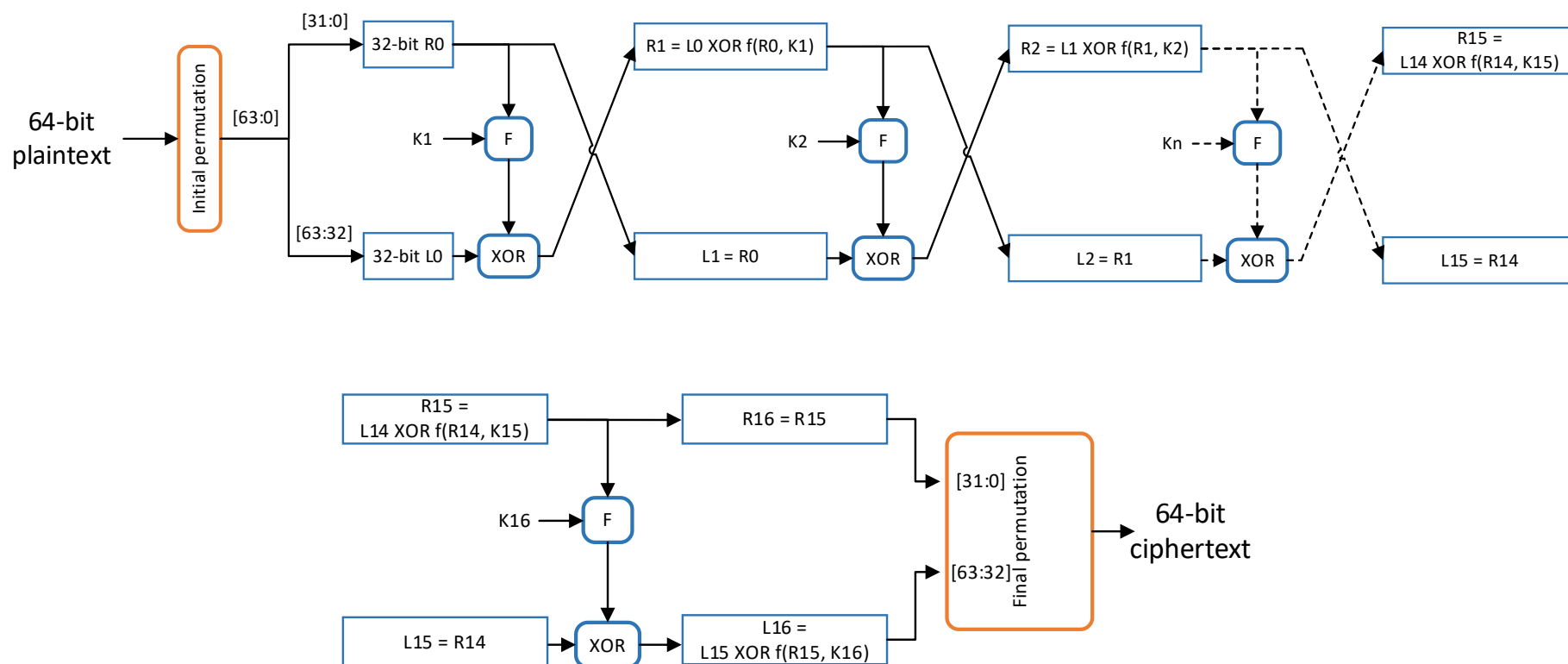
- Details of F function is on the next slide




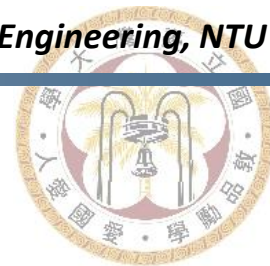

F Function

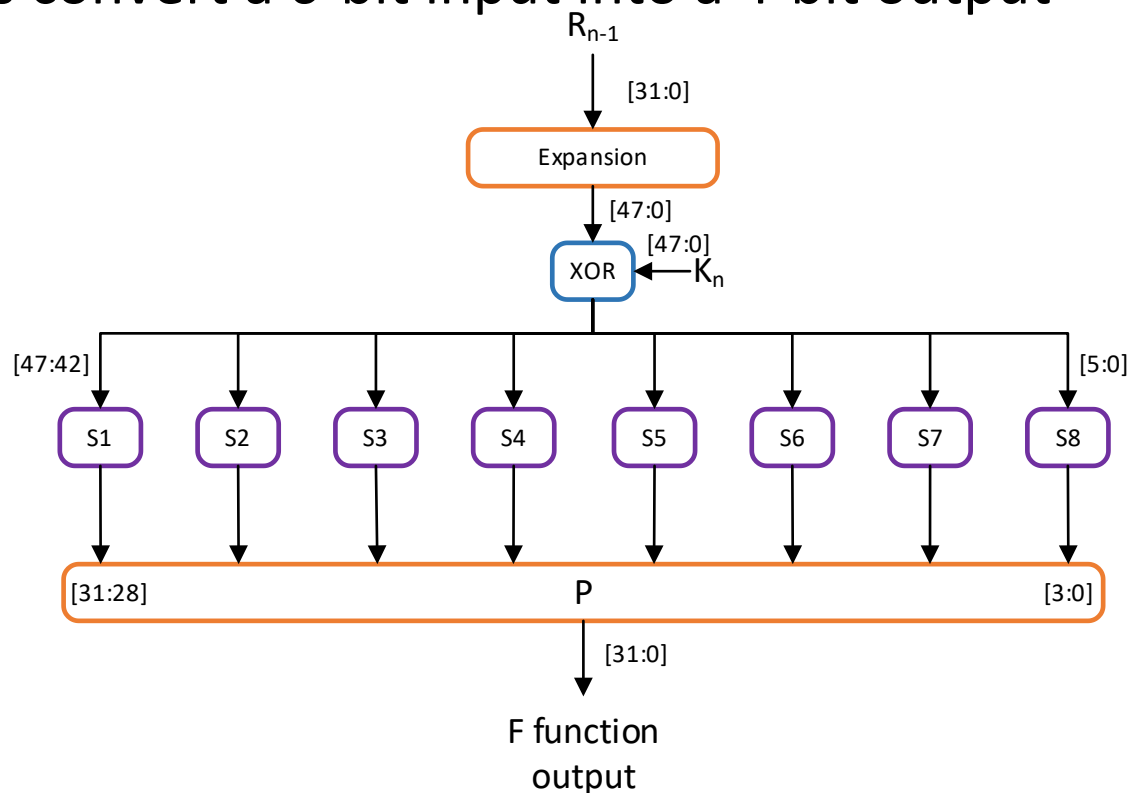- The Expansion LUT transforms a 32-bit input into a 48-bit output
- S-boxes convert a 6-bit input into a 4-bit output



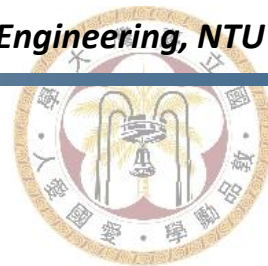

S-box

- Excel files for S1 to S8 are located in the 'S_boxes' folder
- The method of S-box reading is as follows

6-bit input data
 Row number 1 1 0 0 1 0
 1 y y y y 0 Column number
 x 1 0 0 1 x


	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P	Q
1	S1	x0000x	x0001x	x0010x	x0011x	x0100x	x0101x	x0110x	x0111x	x1000x	x1001x	x1010x	x1011x	x1100x	x1101x	x1110x	x1111x
2	0yyyy0	14	4	13	1	2	15	11	8	3	10	6	12	5	9	0	7
3	0yyyy1	0	15	7	4	14	2	13	1	10	6	12	11	9	5	3	8
4	1yyyy0	4	1	14	8	13	6	2	11	15	12	9	7	3	10	5	0
5	1yyyy1	15	12	8	2	4	9	1	7	5	11	3	14	10	0	6	13

4-bit output data
 1 1 0 0



F2: Decrypt(N)

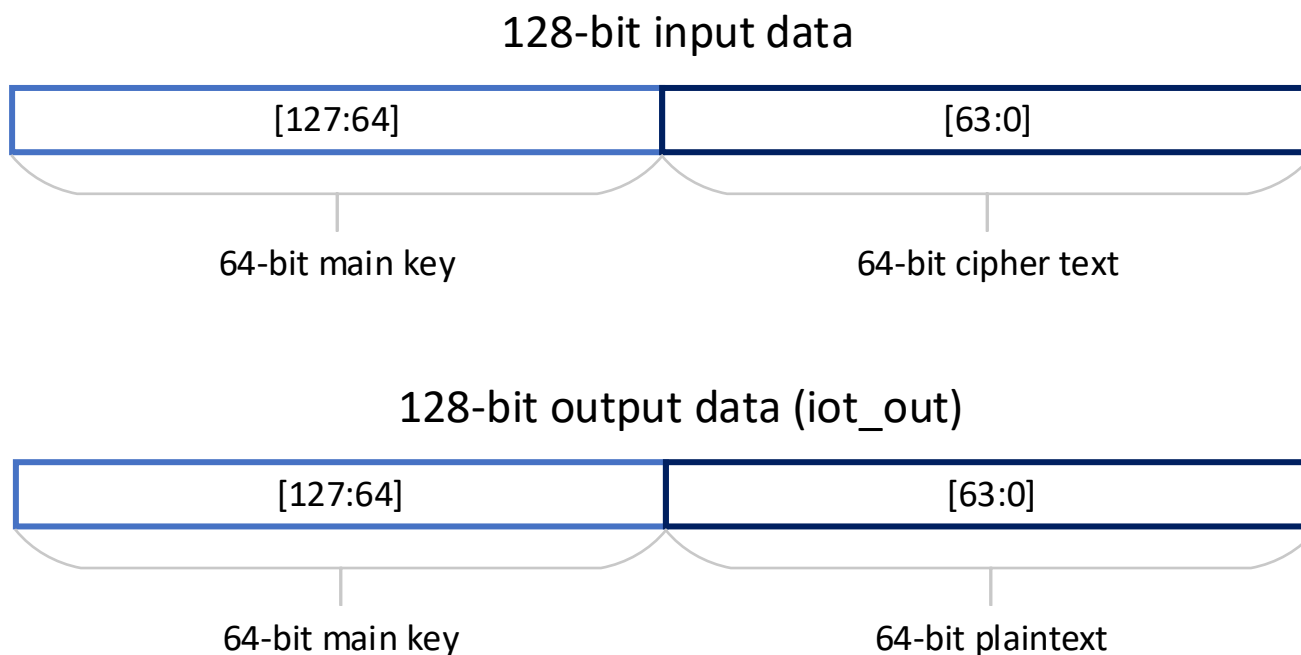- Use the DES algorithm to decrypt 64-bit data
- Operation process is similar to Encrypt, with the only difference being the usage order of the sub-keys, changing from 1~16 to 16~1





F3: CRC_gen(N)

- Generate a CRC checksum [3]
- Generator polynomial = $x^3 + x + 1$
 - This assignment focuses on this Generator polynomial
- Place 3-bit calculation result in `iot_out[2:0]`, and fill the rest with zeros

Assume input data: 1101
 CRC Outcome: `iot_out[2:0]` = 001

$$\begin{array}{r}
 1111 \\
 1011 \overline{) 1101000} \\
 \underline{1011} \\
 1100 \\
 \underline{1011} \\
 1110 \\
 \underline{1011} \\
 1010 \\
 \underline{1011} \\
 001
 \end{array}$$

Note: 4 bit for example



F4: Bin2Gray(N)

- Converts data from binary to gray code [4]

Binary number: $b_nb_{n-1}...b_1b_0$

Gray code: $g_ng_{n-1}...g_1g_0$

Algorithm (\oplus means XOR)

$$g_n = b_n$$

$$g_{n-1} = b_n \oplus b_{n-1}$$

....

$$g_1 = b_2 \oplus b_1$$

$$g_0 = b_1 \oplus b_0$$

Example:

Binary number = 1101

$$g_3 = b_3 = 1$$

$$g_2 = b_3 \oplus b_2 = 0$$

$$g_1 = b_2 \oplus b_1 = 1$$

$$g_0 = b_1 \oplus b_0 = 1$$

Gray code = 1011

Note: 4 bit for example



F5: Gray2Bin(N)

- Converts data from gray code to binary [5]

Binary number: $b_n b_{n-1} \dots b_1 b_0$

Gray code: $g_n g_{n-1} \dots g_1 g_0$

Algorithm (\oplus means XOR)

$$b_n = g_n$$

$$b_{n-1} = g_{n-1} \oplus g_n$$

....

$$b_1 = g_1 \oplus g_2 \oplus g_3 \dots \oplus g_n$$

$$b_0 = g_0 \oplus g_1 \oplus g_2 \oplus g_3 \dots \oplus g_n$$

Example:

Gray code = 1011

$$b_3 = g_3 = 1$$


$$b_2 = g_2 \oplus g_3 = 1$$

$$b_1 = g_1 \oplus g_2 \oplus g_3 = 0$$

$$b_0 = g_0 \oplus g_1 \oplus g_2 \oplus g_3 = 1$$

Binary number = 1101

Note: 4 bit for example

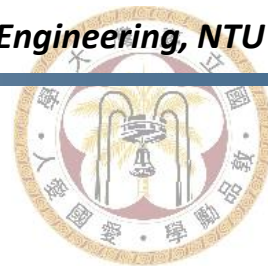

IOTDF.v

```
`timescale 1ns/10ps
module IOTDF( clk, rst, in_en, iot_in, fn_sel, busy, valid, iot_out);
input      clk;
input      rst;
input      in_en;
input [7:0] iot_in;
input [2:0] fn_sel;
output     busy;
output     valid;
output [127:0] iot_out;

endmodule
```



rtl_01.f

- Filelist

```
// -----  
// Simulation: HW4_IOT  
// -----  
  
// testbench  
// -----  
../00_TESTBED/testfixture.v  
  
// design files  
// -----  
./IOTDF.v
```



02_SYN

- IOTDF_DC.sdc

```
# operating conditions and boundary conditions #  
  
create_clock -name clk -period 6.5 [get_ports clk] ;#Modify period by yourself
```

- Run the command to do synthesis
 - syn.tcl needs to be written by yourself (can refer to hw3)

```
dc_shell-t -f syn.tcl | tee syn.log
```



rtl_03.f

- Filelist

```
// -----  
// Simulation: HW4_IOT  
// -----  
  
// testbench  
// -----  
../00_TESTBED/testfixture.v  
/home/raid7_2/course/cvsd/CBDK_IC_Constest_v2.5/Verilog/tsmc13_neg.v  
  
// design files  
// -----  
./IOTDF_syn.v
```



runall_rtl & runall_syn

- runall_rtl

```
vcs -f rtl_01.f -full64 -R +v2k -sverilog -v2005 \  
-debug_access+all +define+p1+F1 | tee rtl_F1.log
```

- runall_syn

```
vcs -f rtl_03.f -full64 -R +v2k -debug_access+all \  
+define+SDF+p1+F1 +neg_tchk | tee rtl_syn_F1.log
```




testfixture.v

- P2 is for hidden pattern


```
`timescale 1ns/10ps
`define SDFFILE      "./IOTDF_syn.sdf"      //Modify your sdf file name
`define CYCLE        6.5                    //Modify your CYCLE
`define DEL          1.0
`define PAT_NUM      60
`define End_CYCLE    1000000
```

```
localparam F5_NUM = 60;
`elsif p2 // modify the following number according to your pattern
    localparam PAT_NUM = 60;
    localparam F1_NUM = 60;
    localparam F2_NUM = 60;
    localparam F3_NUM = 60;
    localparam F4_NUM = 60;
    localparam F5_NUM = 60;
```



Submission

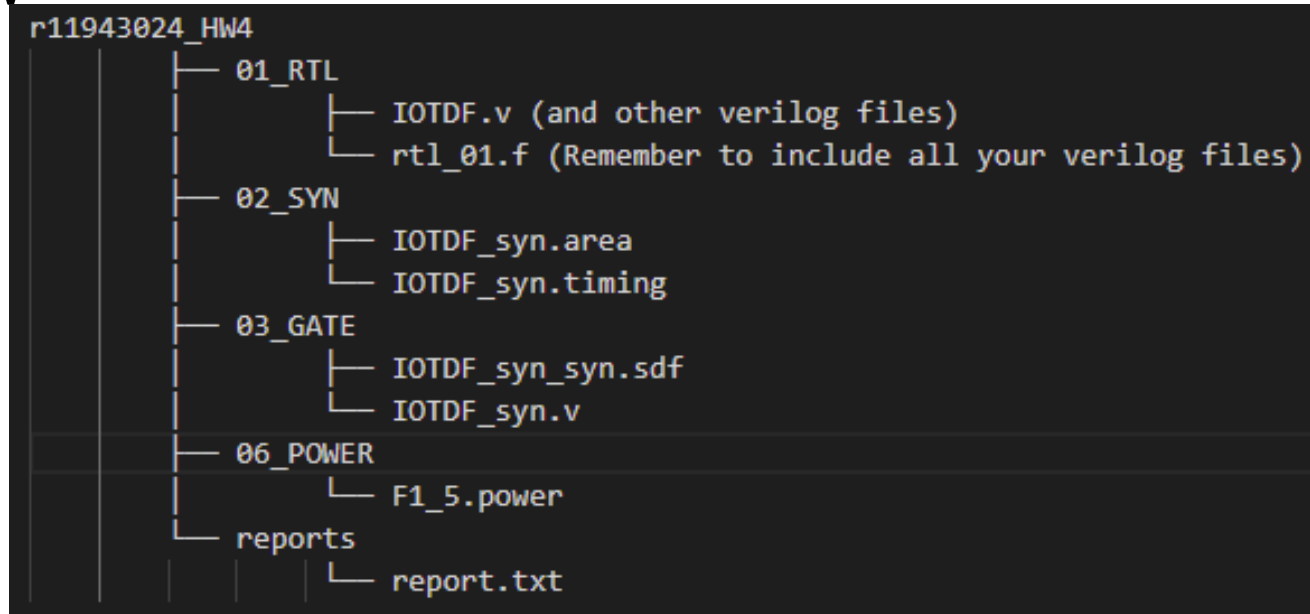- Create a folder named `studentID_hw4` and follow the hierarchy below



- Compress the folder **studentID_hw4** in a tar file named **studentID_hw4_vk.tar** (k is the number of version, $k = 1, 2, \dots$)
- Submit to NTU Cool



Report

- TAs will run your design with the reported clock periods
- report.txt (record the power and processing time of gate-level simulation)

```
StudentID: r11943024
```

```
Clock period: 5.0 (ns)
```

```
Area: 30000.00 (um^2)
```

```
-----  
f1 time: 10016.50 (ns)
```

```
f1 power: 0.9197 (mW)
```

```
-----  
f2 time: 10016.50 (ns)
```

```
f2 power: 0.9197 (mW)
```

```
-----  
f3 time: 10023.00 (ns)
```


```
f3 power: 0.9197 (mW)
```

```
-----  
f4 time: 10023.00 (ns)
```

```
f4 power: 0.9197 (mW)
```

```
-----  
f5 time: 10016.50 (ns)
```

```
f5 power: 0.9197 (mW)
```

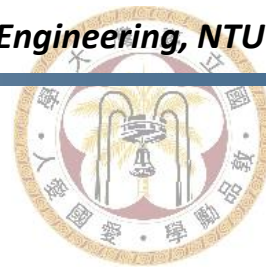

Grading Policy

■ Simulation:

	Score
RTL simulation	40%
Gate-level simulation	20%
Hidden pattern (Gate-level)	10%

■ Performance: (Use pattern1)

- Performance = (Power1 × Time1 + ... + Power5 × Time5) × Area

Unit: Power(mW), Time(ns), Area(um²)

- Baseline = 3×10^{10}
- Need to pass hidden pattern to get the score of this part

	Score
Baseline	10%
Ranking (Need to pass Baseline)	20%



Area

- Area: Cell area from synthesis report (ex. 93677.81 μm^2 below)

```
Library(s) Used:
```

```
slow (File: /home/raid7_2/course/cvsd/CBDK_IC_Contest/CIC/SynopsysDC/db/slow.db)
```

```
Number of ports:                2094
```

```
Number of nets:                 7021
```

```
Number of cells:                5518
```

```
Number of combinational cells:  2275
```

```
Number of sequential cells:     2756
```

```
Number of macros/black boxes:   0
```

```
Number of buf/inv:             245
```

```
Number of references:           543
```

```
Combinational area:            19331.688287
```

```
Buf/Inv area:                  935.267387
```

```
Noncombinational area:         74346.119583
```

```
Macro/Black Box area:          0.000000
```

```
Net Interconnect area:         undefined (No wire load specified)
```

```
Total cell area:               93677.807871
```

```
Total area:                    undefined
```



Time

- Time: processing time from simulation (ex. 6493.50ns below)

```
P55:  ** Correct!!  ** , iot_out=4f767ba1adb71f94c8fb1345d137a58f
P56:  ** Correct!!  ** , iot_out=1a8e5ea79f4b656e55686cedcf47d37b
P57:  ** Correct!!  ** , iot_out=e2d7c49ad64e0a11b895fc5a1f08b7b5
P58:  ** Correct!!  ** , iot_out=12cad57a543ff9929f59ee6a6e7d4509
P59:  ** Correct!!  ** , iot_out=323ebd4b7832c2dde1202bfabf121766
```

```
-----
Congratulations! All data have been generated successfully!
```

```
Total cost time: 6493.50 ns
```

```
-----PASS-----
```



Power

- Power: Use below command to analyze the power. (Need to source the following .cshrc file first!) (ex. 2.948 mW below)

```
Unix% source /usr/cad/synopsys/ClC/primetime.cshrc  
Unix% pt_shell -f ./pt_script.tcl | tee pp.log
```

```
Net Switching Power = 4.176e-05 ( 1.42%)  
Cell Internal Power = 2.837e-03 (96.24%)  
Cell Leakage Power = 6.923e-05 ( 2.35%)  
-----  
Total Power = 2.948e-03 (100.00%)  
  
X Transition Power = 3.541e-06  
Glitching Power = 0.0000  
  
Peak Power = 2.2013  
Peak Time = 6.500
```



Grading Policy

- TA will use **runall_rtl** and **runall_syn** to run your code at RTL and gate-level simulation.
- Do not memorize the answers directly in any way
- **No delay submission is allowed**
- Lose **5 point** for any wrong naming rule or format for submission
- **No plagiarism**



Hints

- Clock gating
- Register sharing
- Pipelining
- Reasonably use LUT



References

- [1] Reference for IOTDF concept
 - IC Design Contest, 2019.
- [2] Reference for DES algorithm
 - [DES Algorithm - HackMD](#)
- [3] Reference for CRC calculation
 - [On-line CRC calculation and free library - Lammert Bies](#)
- [4] Reference for Bin2Gray
 - [Conversion of Binary to Gray Code
 \(tutorialspoint.com\)](#)
- [5] Reference for Gray2Bin
 - [Conversion of Gray Code to Binary
 \(tutorialspoint.com\)](#)